

Graphic Equalizer

Divyansh verma
23f3000103

Center Frequencies:

100 Hz

1 kHz


10 kHz

Calculation :

Graphic Equalizer : Band Pass Filter

23f3000103

Divyansh Verma

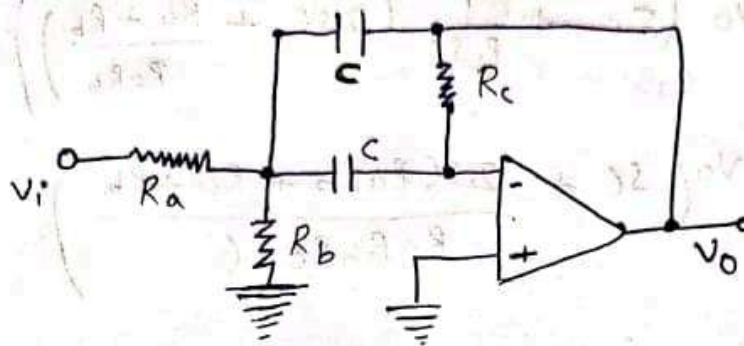

Here, the i through R_c and the capacitor will be same as the input impedance is infinite.

$$\frac{V_o}{R_c} = \frac{0 - V}{1/sC} \quad (\text{Laplace domain})$$

$$\therefore V = \frac{-V_o}{R_c sC} \quad \text{--- (1)}$$

Apply KCL to find V .

$$\therefore \frac{V_i - V}{R_a} + \frac{V_o - V}{1/sC} + \frac{0 - V}{1/sC} + \frac{0 - V}{R_b} = 0$$

$$\frac{V_i}{R_a} + V_o sC = \frac{V}{R_a} + V sC + V sC + \frac{V}{R_b}$$

$$\frac{V_i}{R_a} + V_o sC = V \left(2sC + \frac{1}{R_a} + \frac{1}{R_b} \right)$$

$$\frac{V_i}{R_a} + V_o s C = -\frac{V_o}{R_c s C} \left(2sC + \frac{1}{R_a} + \frac{1}{R_b} \right)$$

$$\frac{V_i}{R_a} = -V_o \left(sC + \frac{1}{R_c s C} \left(2sC + \frac{R_a + R_b}{R_a R_b} \right) \right)$$

$$\frac{V_i}{R_a} = -V_o \left(sC + \frac{2sC R_a R_b + R_a + R_b}{R_a R_b R_c s C} \right)$$

$$\frac{V_i}{R_a} = -V_o \left(\frac{R_a R_b R_c s^2 C^2 + 2sC R_a R_b + R_a + R_b}{R_a R_b R_c s C} \right)$$

$$-\frac{V_o}{V_i} = \frac{R_b R_c s C}{R_a R_b R_c s^2 C^2 + 2sC R_a R_b + R_a + R_b}$$

$$\frac{V_o}{V_i} = \frac{-s/R_a C}{s^2 + \frac{2s}{R_c C} + \left(\frac{1}{R_a} + \frac{1}{R_b} \right) \frac{1}{R_c C^2}}$$

∴ This is transfer function of filter.

Comparing the transfer function with standard transfer function.

$$H(s) = \frac{-A_0 \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$\Rightarrow \omega_0 = \sqrt{\left(\frac{1}{R_a} + \frac{1}{R_b}\right) \frac{1}{R_c C^2}}$$

$$\Rightarrow B = \frac{2}{R_c C}$$

$$\Rightarrow Q = \frac{\omega_0}{B} = \frac{1}{2} \sqrt{R_c \left(\frac{1}{R_a} + \frac{1}{R_b}\right)}$$

$$\Rightarrow A_0 = \frac{-R_c}{2R_a}$$


• Assuming a constant capacitance 'C',

$$R_c = \frac{2Q}{\omega_0 C}$$


$$R_b = \frac{Q}{\omega_0 C (2Q^2 - A_0)}$$

$$R_a = \frac{Q}{A_0 \omega_0 C}$$


LT Spice Circuit:

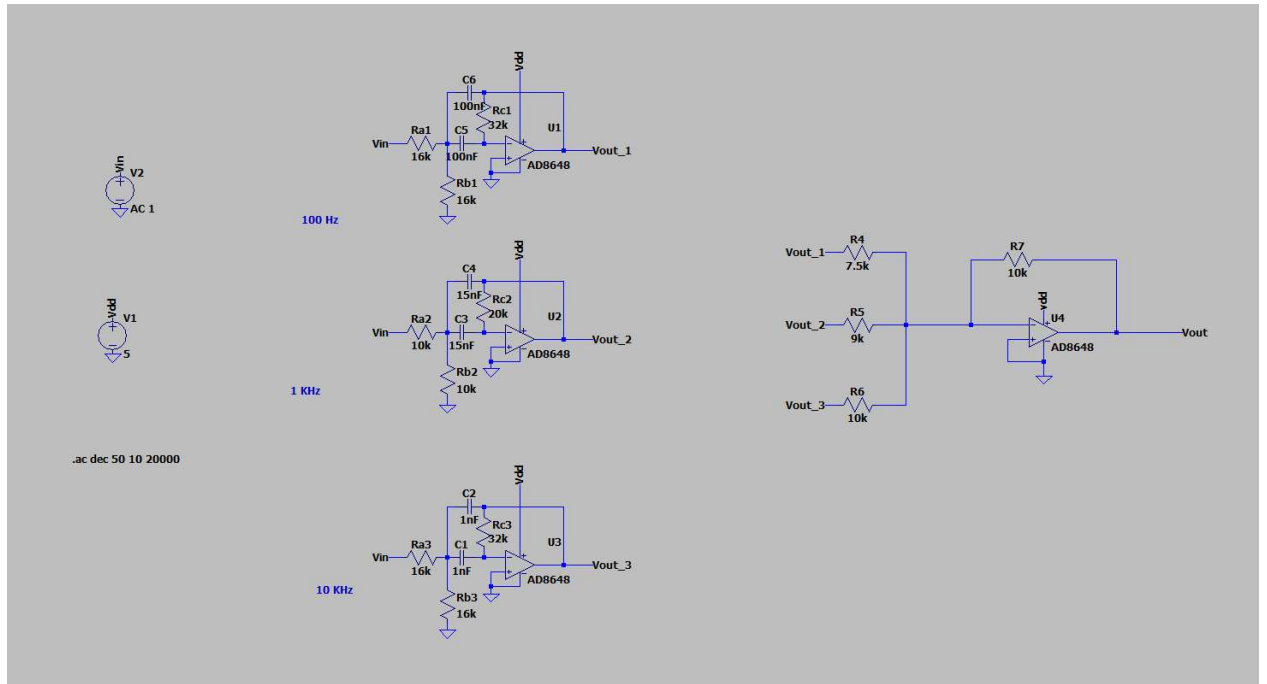

LT Spice - Bode Plot:

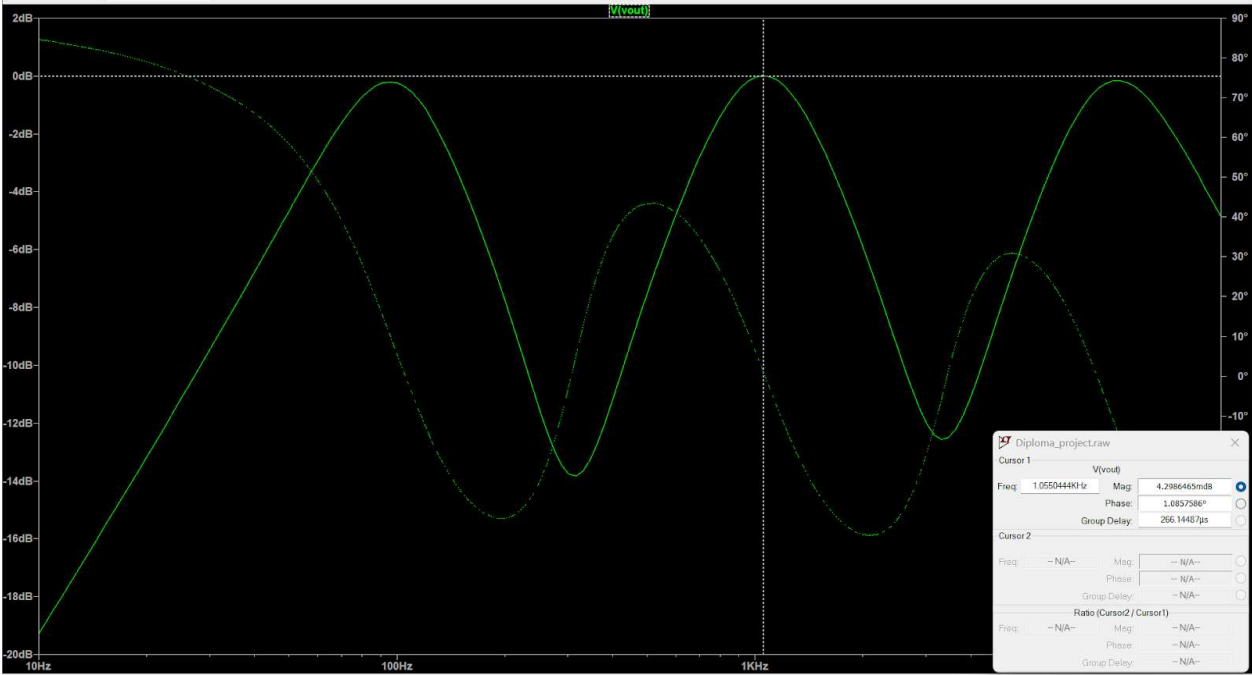

Individual Bandpass Code Plots:

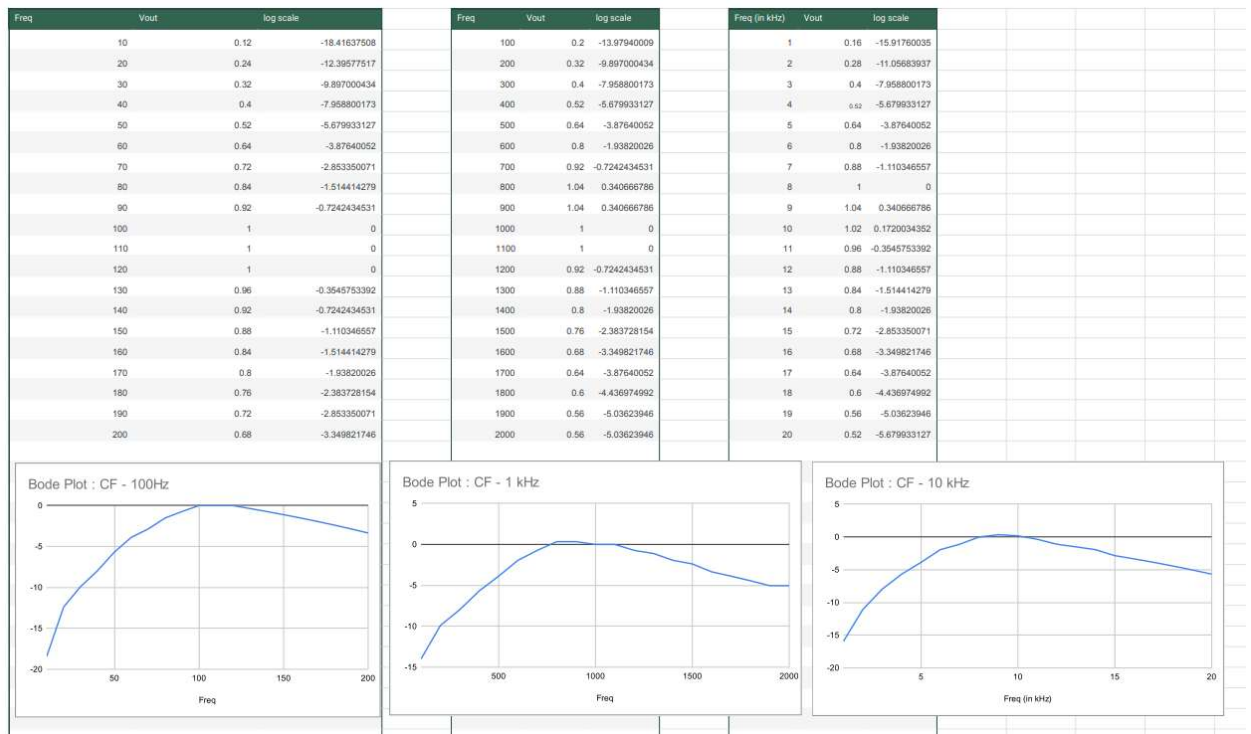


Individual Bandpass Data [Link](#)

Matlab Code:

```
filename = 'Diploma_Project_Bode_plot.csv';
data = readtable(filename);
freq = data.Frequency;
Vin = 1000; %in mV
Vout = data.V_out; %in mV
magnitude_ratio = Vout ./ Vin;
magnitude_dB = 20 * log10(magnitude_ratio);
figure;
semilogx(freq, magnitude_dB, 'b', 'LineWidth', 1.5);
grid on;
title('Bode Plot');
ylabel('Magnitude (dB)');
xlabel('Frequency (Hz)');
```

Bode Plot (with Adder):

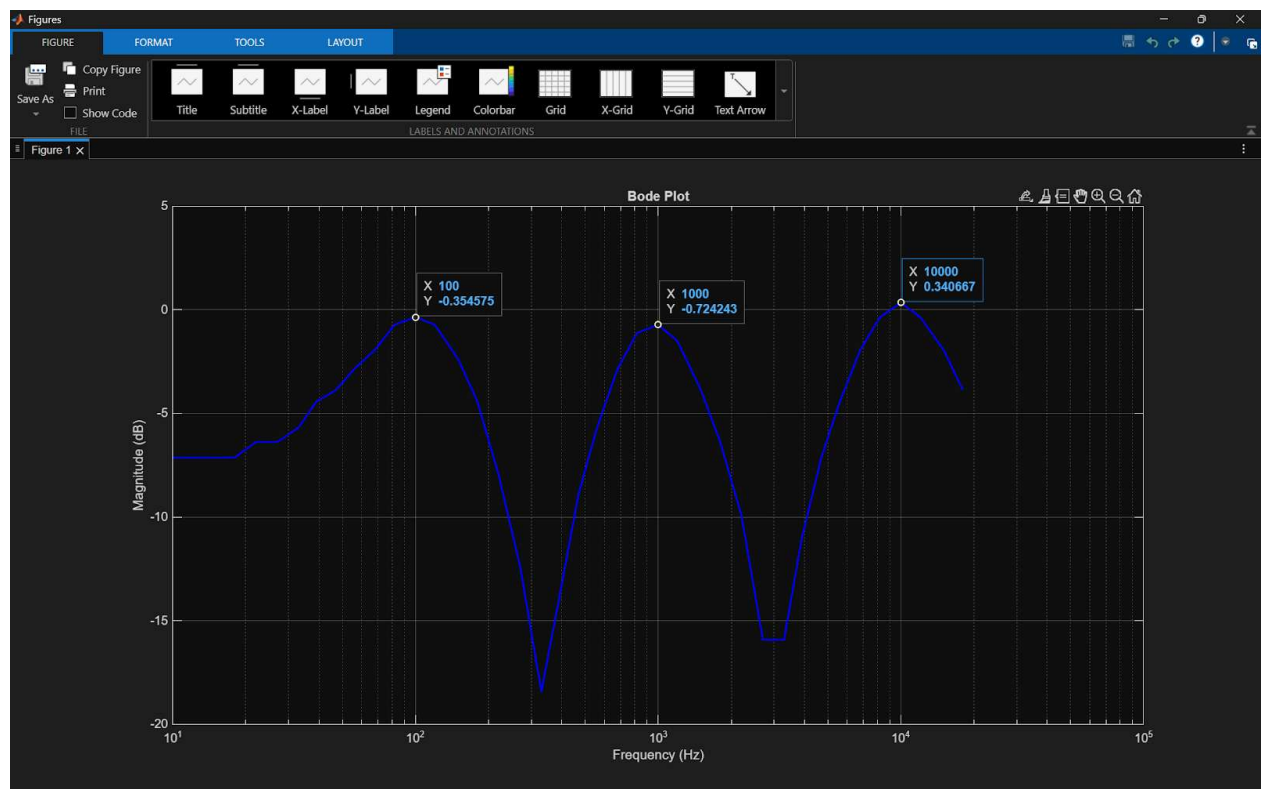

[Data file](#)

Circuit:

